

Electrical Circuit Design using Latex

K Prasanna Kumar and G V V Sharma

CONTENTS

Abstract—This module explains how to draw electrical circuits using latex.

1 INSTALLATION OF LATEX PACKAGE

Installation of all packages at once

```
sudo apt-get install texlive-full
```

Installation or Loading of individual packages

For installing or updating particular package of texlive, we should go with following commands. In the module we make use of 'circuitikz' package, so the following helps to install or load 'circuitikz' into texlive.

```
sudo apt-get install xzdec
```

xzdec is an texlive package manager dependency. Initialize LaTeX package database

```
tlmgr init-usertree
```

Install the *circuitikz* package

```
tlmgr install circuitikz
```

Thus texlive (Latex) package can be installed or loaded.

Documentation main frame

```
\documentclass[12pt]{article}

\usepackage{circuitikz}
\begin{document}


\end{document}
```

First author is an IEEE student member, IEEE Bungle Section, e-mail: k.prasannakumar@ieee.org. Second author is with the Department of Electrical Engineering, IIT, Hyderabad 502285 India e-mail: {gadepall}@iith.ac.in.

2 ANALOG CIRCUITS

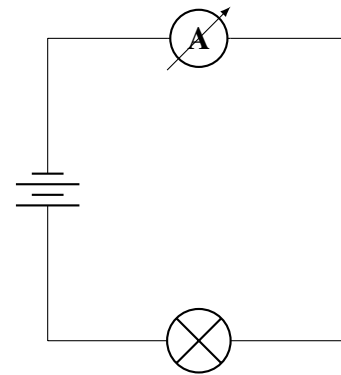2.1 Current Measurement Circuit

```
\begin{center}
\begin{circuitikz} \draw
(0,0) to[battery] (0,4)
to[ammeter] (4,4) -- (4,0)
to[lamp] (0,0)
;
\end{circuitikz}
\end{center}
```




Description ::

- The first line "(0,0) to[battery] (0,4)" says that place a battery in between (0,0) & (0,4)
- The second line "(4,4) to[battery] (4,0)" says that place an ammeter in between (4,4) & (4,0) and Draw a line form (4,4) to (4,0)
- The third line "(4,0) to[battery] (0,0)" says that place lamp in between (4,0) & (0,0)

2.2 Voltage Measurement Circuit


```
\begin{center}
\begin{circuitikz}
\draw
(0,0) to[battery] (0,4) -- (2,4)
to[lamp] (2,0) -- (4,0)
to[voltmeter] (4,4) -- (2,4)
(2,0) -- (0,0);
\end{circuitikz}
```

```
\end{center}
```

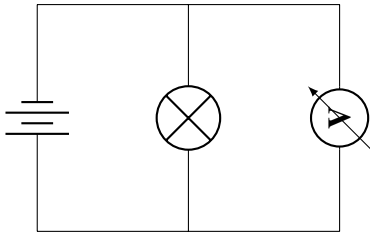

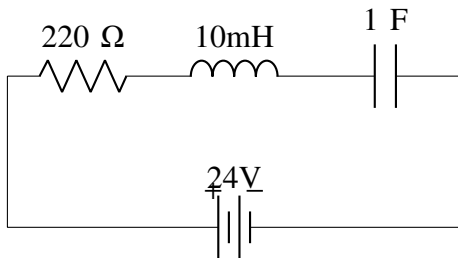
2.3 RLC Circuit

```
\begin{center}
\begin{circuitikz}
\draw
(0,0) to[battery] (6,0) -- (6, 2)
(0,0) -- (0,2) to[R = 220 \ohm]
(2,2) to[L = 10 mH] (4,2) to[C =
1 F] (6,2) -- (6,0) ;
\end{circuitikz}
\end{center}
```




Circuit with bipoles can be drawn using above syntax. But for monopoles and multipoles the following syntax should be used
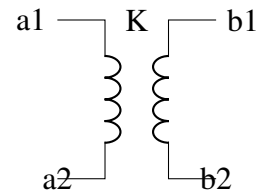
```
\begin{center}
\begin{circuitikz}
\draw
(0,0) node[transformer] (T) {}
(T.A1) node[anchor = east] {a1}
(T.A2) node(anchor = east) {a2}
(T.B1) node[anchor = west] {b1}
(T.B2) node(anchor = west) {b2}
(T.base) node{K}
;
\end{circuitikz}
\end{center}
```



2.4 Half Wave Rectifier Circuit


```
\begin{center}
\begin{circuitikz}
\draw
(0,2) node[transformer] (T1){}
(T1.A1) to[sinusoidal voltage
source] (T1.A2)
(T1.B1) to[diode] (3, 2) to[R]
(3,0) |- (T1.B2)
;
\end{circuitikz}
\end{center}
```

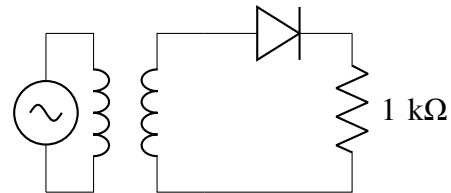

3 DIGITAL CIRCUITS

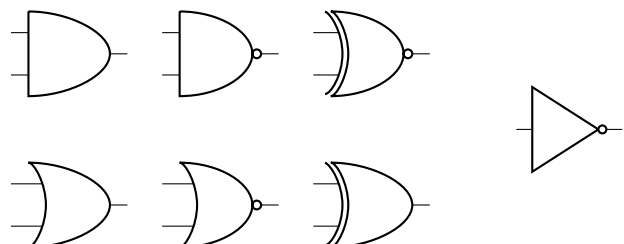3.1 Basic Gates

```
\begin{center}
\begin{circuitikz}
\draw
(4,0) node[xor port]{}
(4,2) node[xnor port]{}
(2,0) node[nor port]{}
(2,2) node[nand port]{}
(0,0) node[or port]{}
(0,2) node[and port]{}
(6,1) node[not port]{}
;
\end{circuitikz}
\end{center}
```




3.2 Logic Circuit

```

\begin{center}
\begin{circuitikz}
\draw
  (0,2) node[nand port] (nand4) {}
  (2,3) node[nand port] (nand3) {}
  (4,2) node[nand port] (nand2) {}
  (0,0) node[nand port] (nand1) {}
  (nand1.out) |- (nand2.in 2)
  (nand4.out) |- (nand3.in 2)
  (nand3.out) |- (nand2.in 1)
  (nand1.in 1) node[anchor = east
    ] {a}
  (nand1.in 2) node[anchor = east
    ] {b}
  (nand3.in 1) node[anchor = east
    ] {c}
  (nand4.in 1) node[anchor = east
    ] {x}
  (nand4.in 2) node[anchor = east
    ] {y}
  (nand2.out) node[anchor = west]
    {output}

;
\end{circuitikz}
\end{center}

```

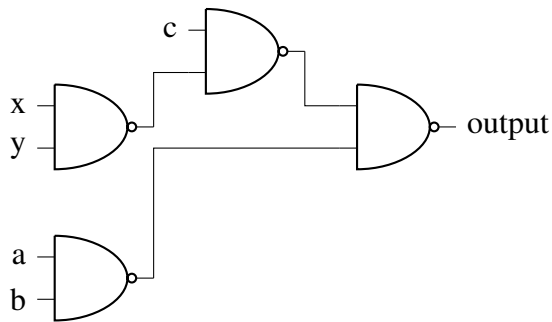

4 FET TRANSISTOR LOGIC

```


\begin{center}
\begin{circuitikz}
\draw
  (0,3) node[pmos, emptycircle] (P1)
    {}
  (0,1) node[nmos](N1) {}
  (P1.drain) -- (N1.drain)
  (P1.source) node[vcc] {5V}
  (N1.source) node[ground](G) {GND}

```

```

(P1.gate) |- (N1.gate)
(-2,2) -- (-1,2) node[inputarrow]
  (inr1){}
(inr1.1) node[anchor = east] {A}
(0,2) -- (1,2) node[inputarrow] (
  inr2){}
(inr2.1) node[anchor = east] {A'}
;
\end{circuitikz}
\end{center}

```

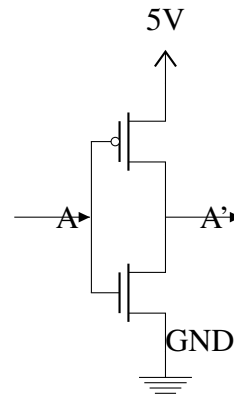


5 SIGNAL FLOW GRAPH

```

\begin{center}
\begin{circuitikz}
\draw
  (0,0) to[vco] (1,0) to[adc] (3,0)
    to[dsp] (5,0) to[dac] (7,0) node
    [txantenna] {TX}
  (1.5,-3.5) to[dac] (3.25,-3.5) to[
    dsp] (5,-3.5) to[adc] (6.5,-3.5)
    node[rxantenna] {RX}
  (1.5, -3.5) node[inputarrow,
    rotate = 180] (inr) {}
  (inr.1) node[anchor = east] {
    output}

;
\end{circuitikz}
\end{center}

```

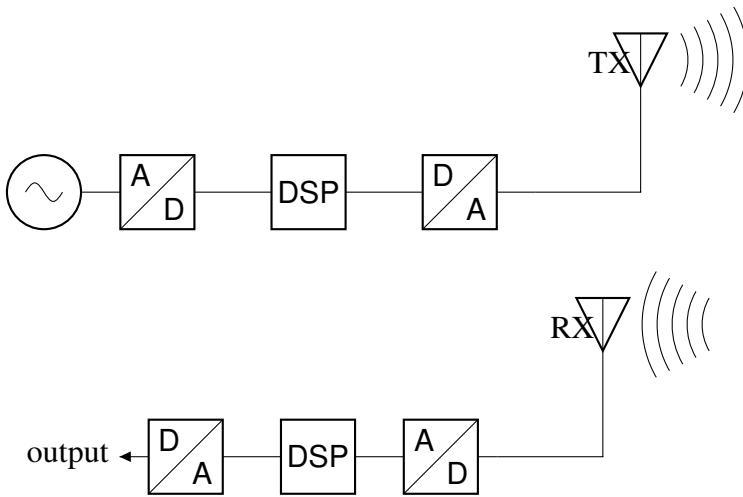


6 CONTROL SYSTEM

```

\begin{center}
\begin{circuitikz}
\draw
(0,0) to[vco] (1,0)
(2,0) node[mixer] (M) {}
(M.1) -- (1,0)
(M.3) to[twoport, t= $\frac{s+4}{s^2+2s+8}$] (5,0) --(6,0)
node[inputarrow] {}
(5,0) -- (5,-2) to[twoport, t = $\frac{1}{s+1}$] (2,-2) -- (M.2)
(M.1) node[inputarrow] {}
(M.2) node[inputarrow, rotate =90] {}
(M.1) node[anchor = west] {+}
(M.2) node[anchor = south] {+}
;
\end{circuitikz}
\end{center}

```

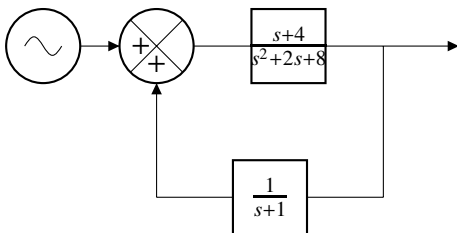

REFERENCES

- [1] Electric Circuit Design <https://github.com/PrasannaIITH/circuitikz>